
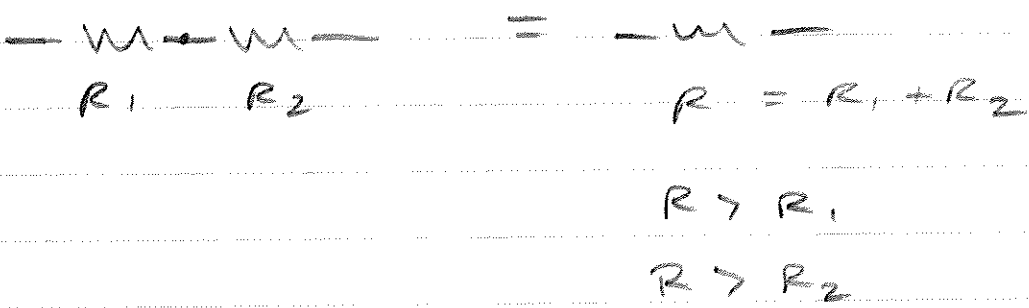


# LEC 15 (PT 1)
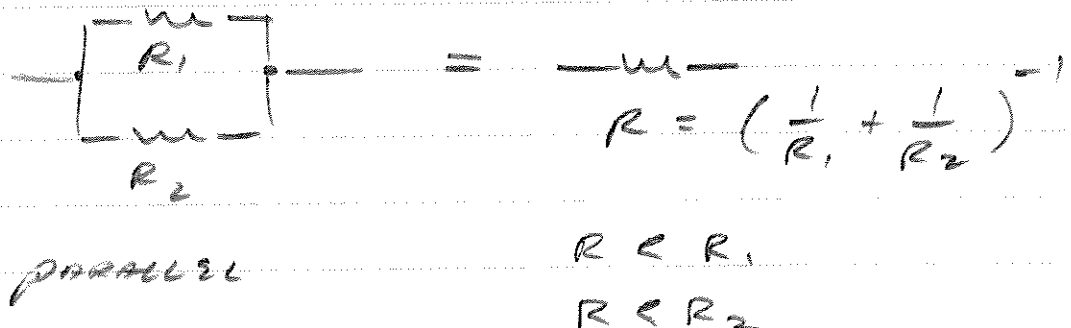
## RESISTORS IN SERIES & PARALLEL + CIRCUITS

AS W/ CAPACITORS WE CAN CONNECT  
RESISTORS IN SERIES + PARALLEL:



CONCEPTUALLY:


• PARALLEL: WE PROVIDE MULTIPLE  
PATHS FOR CURRENT TO FLOW,  
SO RESISTANCE DECREASES.

• SERIES: THE VOLTAGE ACROSS EITHER  
RESISTOR IS LESS THAN  $V$ , THE TOTAL  
VOLTAGE. SO CURRENT IS REDUCED:  $R$  INCREASES.


(2)

## PARALLEL COMBO

TO SEE THAT

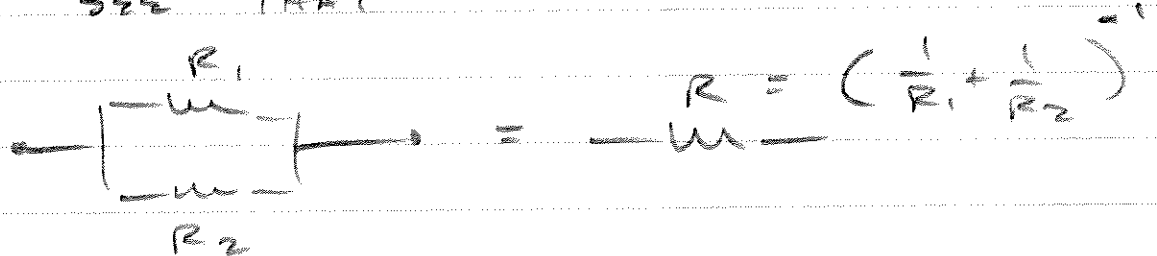

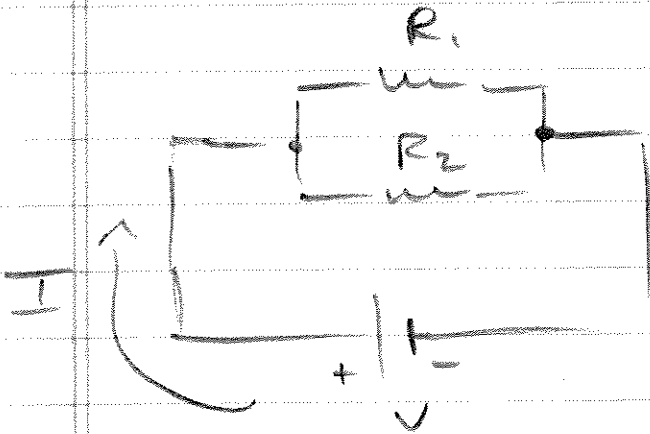
WE APPLY A VOLTAGE  $V$  ACROSS  
THE PARALLEL COMBO &  
DETERMINE THE CURRENT  $I$   
THAT ENTERS THE COMBO:



- THE PARALLEL RESISTANCE IS THEN

$$R = \frac{V}{I}$$

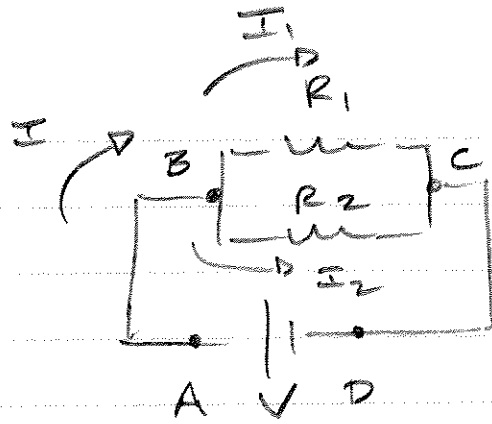- TO DETERMINE  $I$ , WE RECOGNIZE THAT THE VOLTAGE ACROSS EACH RESISTOR IS  $V$ :



VOLTAGE ACROSS  $R_1$  :

$$V_1 = V_B - V_C = V_A - V_D = V$$

(  $V_A = V_B$  &  $V_C = V_D$  since VOLTAGE DROP OVER A WIRE, i.e. A CONDUCTOR, IS ZERO )

LIKEWISE:

$$V_2 = V$$

- By OHM'S LAW, CURRENT THROUGH  $R_1$  IS :

$$I_1 = V_1 / R_1 = V / R_1$$

$$I_2 = V_2 / R_2 = V / R_2$$

- THE TOTAL CURRENT FLOWING INTO THE PARALLEL COMBINATION IS THEREFORE THE SUM  $I_1 + I_2$

$$I = I_1 + I_2 = V / R_1 + V / R_2$$

$$= V \cdot ( 1 / R_1 + 1 / R_2 )$$


- TO DETERMINE R, WE DO IT BY I

$$R = \frac{V}{I} = \frac{V}{\left( V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \right)}$$

$$= \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

- AS WE CLAIMED ON PAGE ①

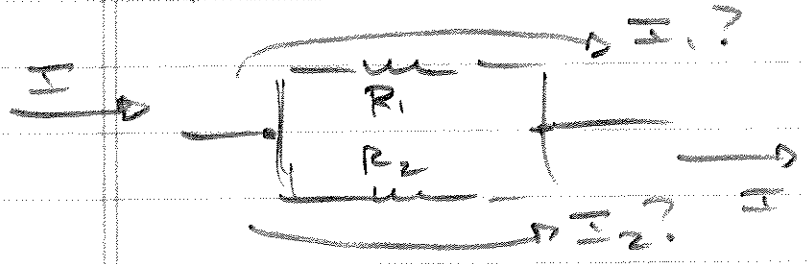- SO HOW IS CURRENT SPLIT UP WHEN IT IS SENT THROUGH A PARALLEL RESISTANCE?



- WELL, VOLTAGE DROP ACROSS  $R_1$  MUST EQUAL VOLTAGE DROP ACROSS  $R_2$

$$V_1 = V_2$$

$$I_1 R_1 = I_2 R_2$$


$$\rightarrow \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

• CURRENT, THEN, IS HIGHER THROUGH THE SMALLER RESISTANCE!

"CURRENT TAKES PATH OF LEAST RESISTANCE"

• APPLICATION: VOLTMETERS

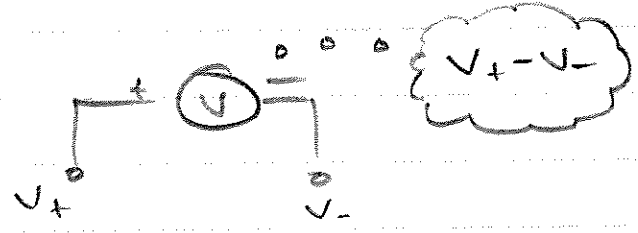
• VOLTMETER IS TWO TERMINAL DEVICE THAT MEASURES THE VOLTAGE DIFFERENCE BETWEEN ITS TWO TERMINALS:





• ELECTRICALLY, IT LOOKS LIKE A RESISTOR:



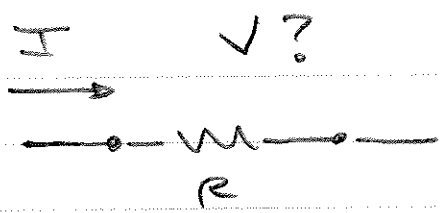• A COMMON APPLICATION IS WHERE A FIXED CURRENT IS CONDUCTING ACROSS A RESISTOR AND WE WANT TO MEASURE THE VOLTAGE ACROSS THE RESISTOR:



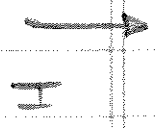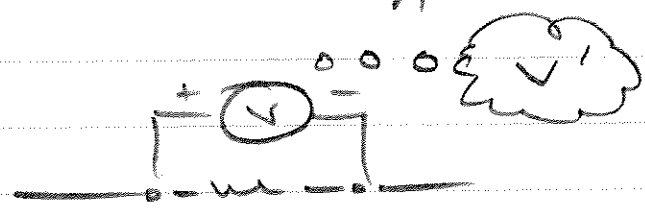• To do this, we connect the voltmeter across the resistance:



• AN OBTAIN A READING  $V'$

• IN GENERAL,  $V' \neq V$ , SINCE THE VOLTMETER HAS SOME RESISTANCE AND WILL DIVERT SOME OF THE TOTAL CURRENT.

• THE CURRENT <sup>I'</sup> THROUGH R WILL THEN IN GENERAL BE LESS THAN I, SO

THAT:

$$V' = I'R < IR = V$$

i.e.  $V' < V$

• THEREFORE, WE WANT TO DESIGN VOLTMETERS TO HAVE VERY LARGE RESISTANCES SO THAT THEY DIVERT MINIMAL CURRENT, AND THUS GIVE AN ACCURATE READING (i.e.  $V' \approx V$ )