

①

Lecture 16 - Kirchoff's Rules & RC Circuits

Summary

- Kirchoff's Voltage Rule:
The sum of the voltage drops across any two paths w/ the same start & end points is the same.
- Kirchoff's Current Rule:
The current entering a junction equals the current exiting.
- Capacitor Current: The increase in charge ΔQ due to a current I charging a capacitor for a time Δt is:

$$\Delta Q = I \Delta t$$


- A capacitor w/ capacitance C charges / discharges through a resistor w/ resistance R w/ a characteristic "time constant" $\tau = RC$

CHARGING: $V(t) = V(1 - e^{-t/\tau})$
 DISCHARGING: $V(t) = V e^{-t/\tau}$


- IN "STEADY STATE" (ALL CURRENTS/VOLTAGES SETTLE TO STEADY VALUES), NO CURRENT ENTERS/EXITS A CAPACITOR AND IT LOOKS LIKE AN OPEN CIRCUIT.

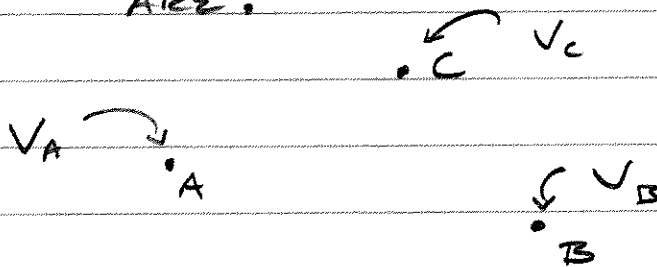16.1 KIRCHOFF'S CIRCUIT RULES

- ELECTRIC POTENTIAL IS A PROPERTY OF WHERE YOU ARE:



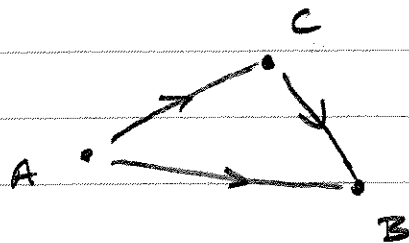- THEN THE DIFFERENCE IN ELECTRIC POTENTIAL BETWEEN TWO ENDS OF A PATH DEPENDS ONLY ON THE END POINTS AND NOT ON THE POINTS IN BETWEEN:



$$\Delta V (A \rightarrow B) = V_A - V_B$$


$$\Delta V (A \rightarrow C \rightarrow B) = \Delta V (A \rightarrow C) + \Delta V (C \rightarrow B)$$

$$= [V_A - V_C] + [V_C - V_B]$$

$$= V_A + [-V_C + V_C] - V_B$$

$$= V_A - V_B = \Delta V (A \rightarrow B)$$

• IN A CIRCUIT, E.G.

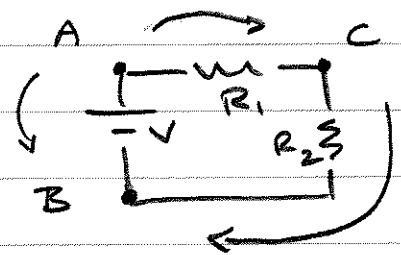

$$\Delta V (A \rightarrow B) = \Delta V (A \rightarrow C \rightarrow B)$$

$$= \Delta V (A \rightarrow C) + \Delta V (C \rightarrow B)$$

$$V = V_1 + V_2$$

"THE VOLTAGE DROP OVER R₁ PLUS THE VOLTAGE DROP OVER R₂ EQUALS THE VOLTAGE DROP OVER THE SOURCE V."


IN GENERAL :

KIRCHHOFF'S VOLTAGE LAW (KVL)

"THE SUM OF THE VOLTAGE DROPS ACROSS ANY TWO PATHS W/ THE SAME START & END POINTS ARE EQUAL."

• WE HAVE IMPLICITLY USING KVL ALREADY :

PARALLEL RESISTORS :

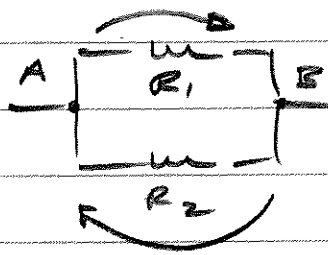

$$\Delta V(A \rightarrow A) = \Delta V(A \rightarrow B \rightarrow A)$$
$$0 = V_1 + (-V_2)$$


(ARROW IS BACKWARDS!)

$$\rightarrow V_2 = V_1$$

"VOLTAGE ACROSS PARALLEL RESISTORS ARE EQUAL"

5

SERIES RESISTORS:

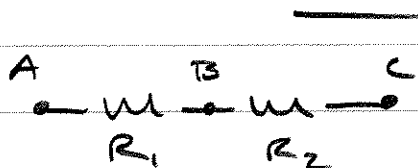

$$\begin{aligned}\Delta V (A \rightarrow C) &= \Delta V (A \rightarrow B \rightarrow C) \\ \Delta V &= \Delta V (A \rightarrow B) + \Delta V (B \rightarrow C) \\ \text{(VOLTAGE ACROSS SERIES)} &= V_1 + V_2\end{aligned}$$

$$\rightarrow V = V_1 + V_2$$

"VOLTAGE ACROSS SERIES COMBINATION IS SUM OF VOLTAGE ACROSS EACH."

PHYSICAL ORIGIN OF KVL:

- $\oint V = \Delta \text{ POT. ENERGY}$
- BUT WE COULD ONLY DEFINE POTENTIAL ENERGY WHEN FORCES WERE CONSERVATIVE
 \rightarrow ENERGY CONSERVATION


• KVL IS A CONSEQUENCE OF ENERGY CONSERVATION!

KIRCHHOFF'S CURRENT LAW (KCL):

- KVL IS CONSEQUENCE OF ENERGY CONSERVATION
- KCL IS " " " " CHARGE " !

KCL: " THE CURRENT ENTERING A JUNCTION EQUALS THE CURRENT EXITING THE JUNCTION "


E.G.

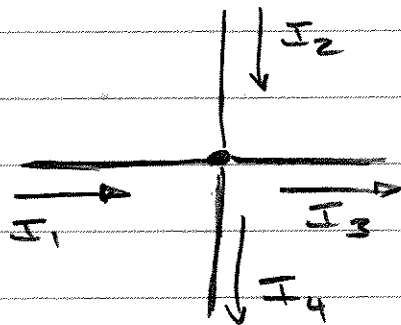

$$I_1 + I_2 = I_3 + I_4$$


- AGAIN, WE HAVE BEEN USING THIS RULE IMPLICITLY ALREADY:

PARALLEL RESISTORS:

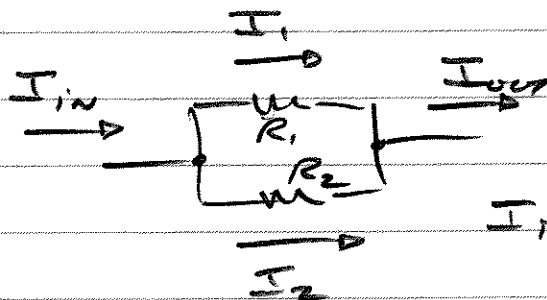

$$I_{IN} = I_1 + I_2 = I_{OUT}$$

SERIES RESISTORS

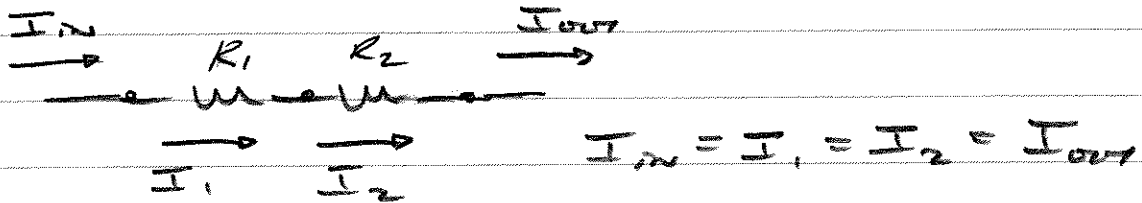



- BUT! CHARGE CONSERVATION ONLY TELLS US THAT CHARGE CAN NOT BE CREATED OR DESTROYED.

- WHY DO WE REQUIRE



- CAN'T WE HAVE CHARGE BUILDING UP / ACCUMULATING IN SOME REGION?



E.G.

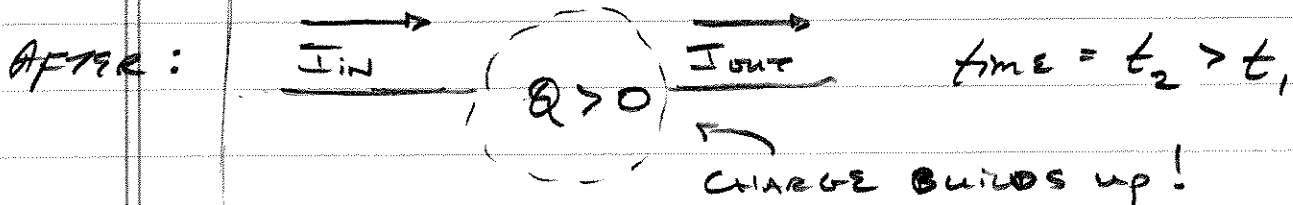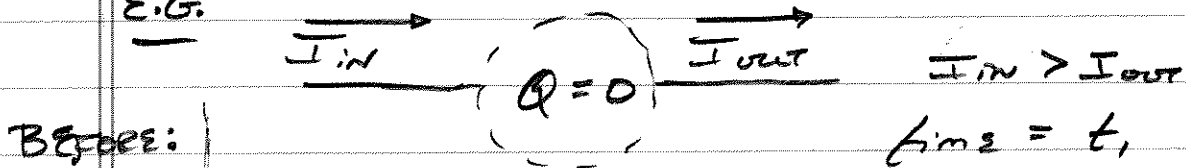

- ANSWER: YES, BUT WE ALREADY HAVE A CIRCUIT ELEMENT THAT STORES CHARGE: A CAPACITOR!

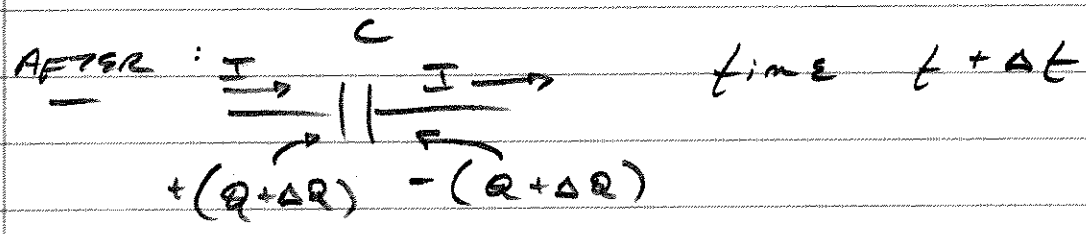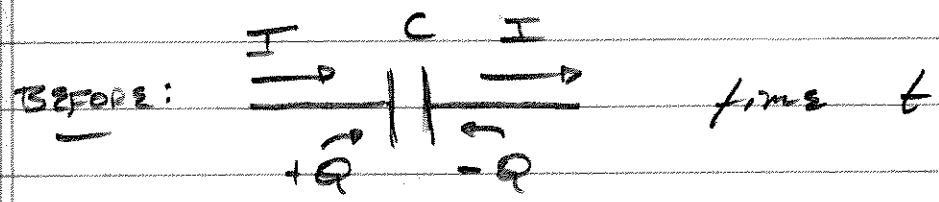16.2: RC CIRCUITS

- LIKE WE CAN HAVE CURRENT THROUGH RESISTORS, WE CAN HAVE CURRENT CHARGING / DISCHARGING A CAPACITOR:



BUT SINCE I IS $\frac{\Delta Q}{\Delta t}$:

$$\Delta Q = I \Delta t$$

QUESTION: TWO CAPACITORS C_1 + C_2 , INITIALLY UNCHARGED, ARE CHARGED BY THE SAME CURRENT I FOR A TIME Δt . IF $C_2 > C_1$, WHICH CAPACITOR HAS THE HIGHER VOLTAGE?

ANSWER: $\Delta Q_1 = I \Delta t = \Delta Q_2$


BUT $V = Q/C$ FOR CAPACITORS SO:

$$\Delta V_1 = \frac{\Delta Q_1}{C_1} = \frac{I \Delta t}{C_1} > \frac{I \Delta t}{C_2} = \frac{\Delta Q_2}{C_2} = \Delta V_2$$

$\rightarrow \Delta V_1 > \Delta V_2$

• CHARGING A CAPACITOR THROUGH A RESISTOR:

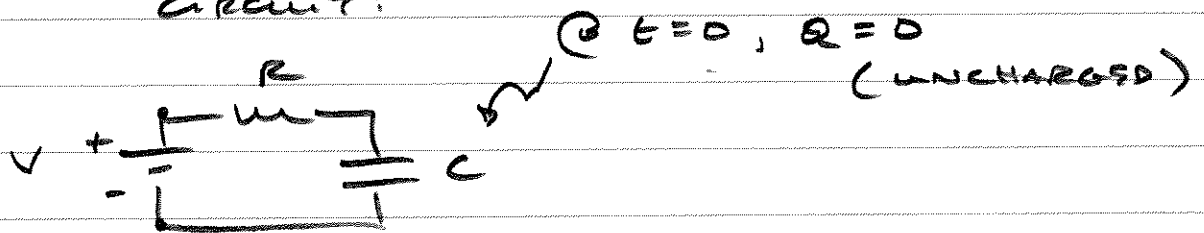• Suppose @ a time $t = 0$
 WE HAVE THE FOLLOWING
 CIRCUIT:



• WHAT HAPPENS FOR $t > 0$?

• BY KVL:

$$V = V_R + V_C$$

@ $t = 0$, THOUGH, $Q = 0$ SO $V_C = 0$

$\rightarrow V_R = V$ (@ $t = 0$)

• By OHM'S LAW :


$$I = \frac{V}{R} \\ = \frac{V}{R} \text{ [@ } t = 0 \text{]}$$

• By KCL :

• CURRENT THROUGH RESISTOR IS SAME CAPACITOR [THEY ARE IN SERIES] .

• THEREFORE @ $t = 0$ CAPACITOR BEGINS CHARGING @ RATE $I = \frac{V}{R}$
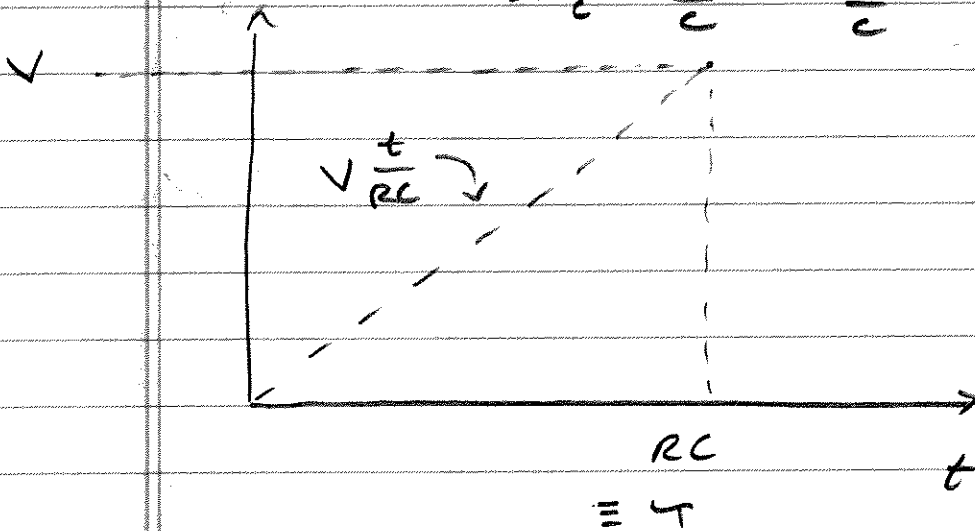
$$\Delta V_c = \frac{\Delta Q}{C} = \frac{I \Delta t}{C} = V \frac{\Delta t}{RC}$$




← "time constant"

• IF IT CONTINUES CHARGING @ THIS RATE, WILL REACH BATTERY VOLTAGE V IN A TIME $t = RC$, CALLED THE "time constant" OF THE CAPACITOR / RESISTOR COMBO.

- AS THE CAPACITOR CHARGES, THE VOLTAGE ACROSS IT INCREASES, WHICH, BY KVL, DECREASES THE VOLTAGE ACROSS THE RESISTOR

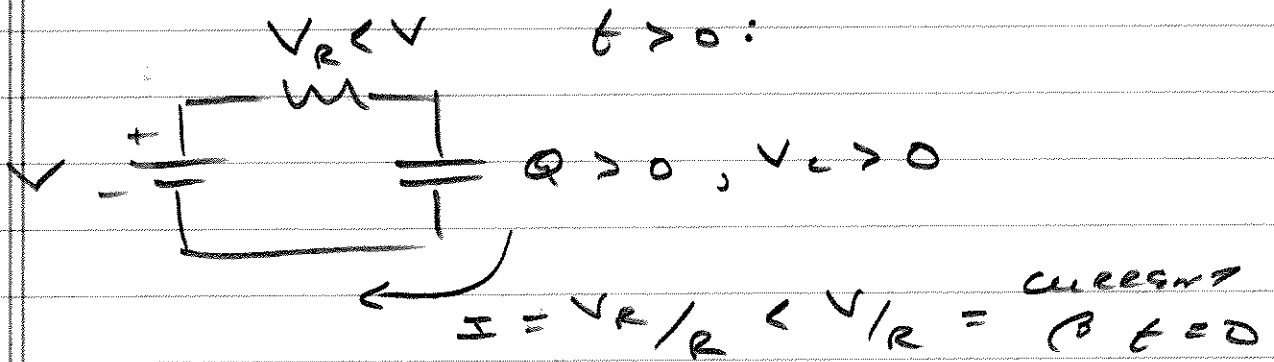- THIS DECREASES THE CURRENT THROUGH THE RESISTOR, WHICH, BY KCL, DECREASES THE RATE β WHICH WE CHARGE THE CAPACITOR:



- AFTER A LONG TIME, WHEN WE REACH STEADY STATE (ALL VOLTAGES STEADY), THE CURRENT GOES TO ZERO (OTHER V_C WOULD BE CHANGING IN TIME).

- IF $I = 0 \rightarrow V_R = 0$ (OHM'S LAW)

- IF $V_R = 0 \rightarrow V_C = V$ (KVL)

NOTE: SINCE IN STEADY STATE THE CURRENT INTO A CAP MUST BE ZERO, THEN IN S.S. A CAP ACTS LIKE AN OPEN CIRCUIT.


• PUTTING THIS TOGETHER :

- At $t = 0$ ($Q = 0$), CAP BEGINS CHARGING @ RATE

$$\frac{\Delta V}{\Delta t} = \frac{V}{T}$$

- AS $t > 0$, RATE OF CHARGING GRADUALLY DECREASES.

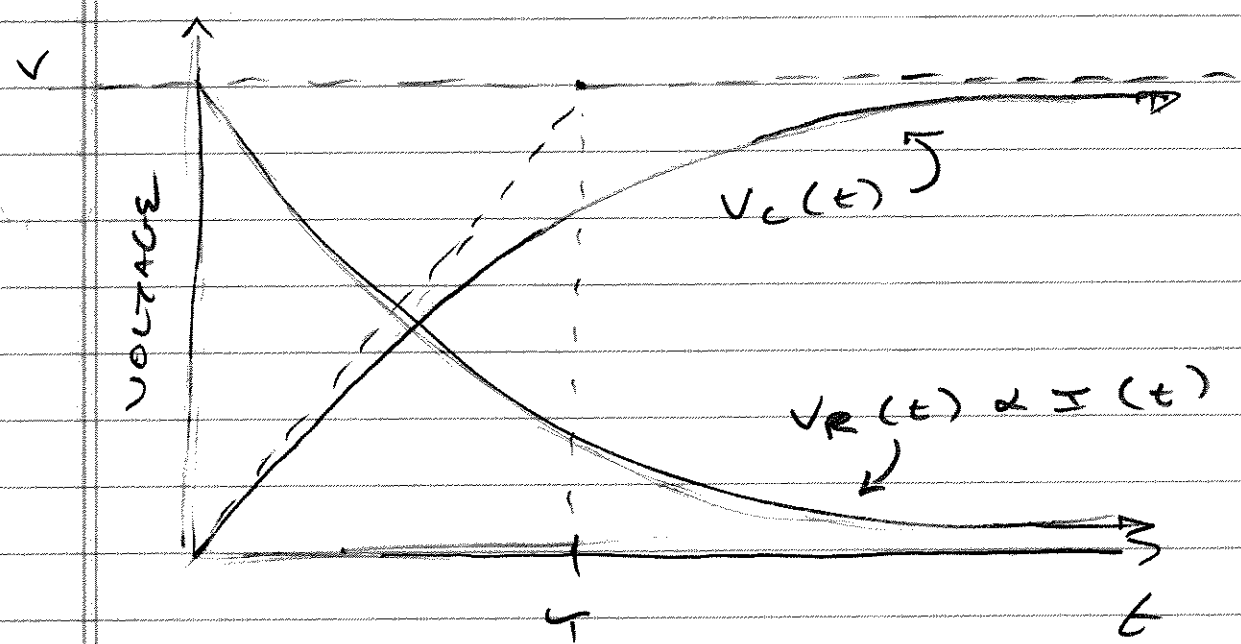- EVENTUALLY, CAPACITOR VOLTAGE SETTLES TO VOLTAGE V OF SOURCE:



• MATHEMATICALLY :

$$V_c(t) = V (1 - e^{-t/T})$$


"EXPONENTIAL CHARGING"

$$V_R(t) = V e^{-t/T}$$

"EXPONENTIAL DECAY"

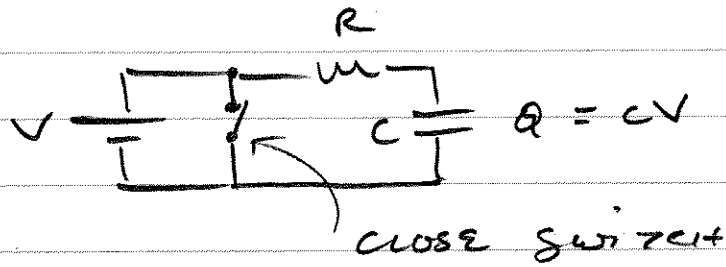• QUESTIONS FOR YOU :

AFTER THE CAPACITOR CHARGES UP TO V , WE "SHORT OUT" THE VOLTAGE SOURCE :



- WHAT HAPPENS TO V_C AFTER WE CLOSE THE SWITCH?
- V_R ?