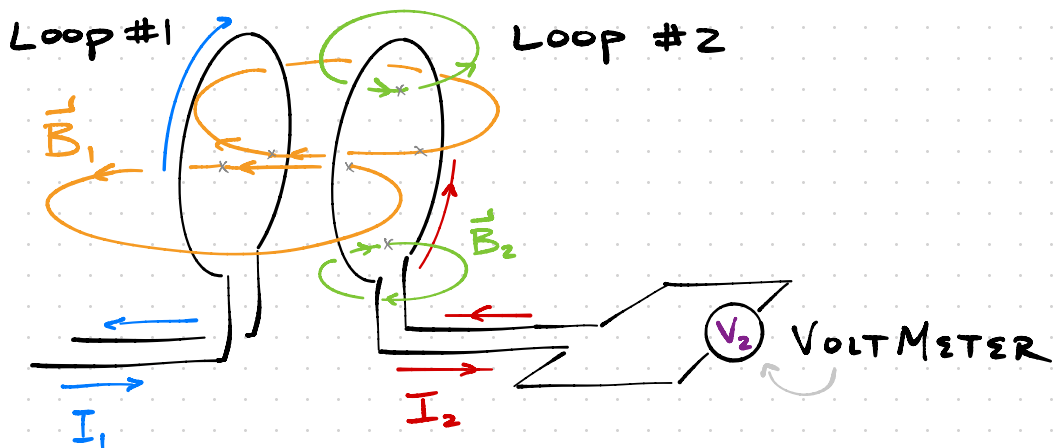


LECTURE 22 NOTES

INDUCTORS + RL
CIRCUITS

• RECAP :

— ELECTROMAGNETIC INDUCTION :



• CHAIN OF INDUCTION :

CHANGING I_1

CHANGING B_1

emf
in Loop #2

CHANGING Φ_2

I_2

V_2

* SEE LECTURE 20 NOTES FOR DETAILS.

- EACH "EFFECT" IN THE CHAIN IS PROPORTIONAL TO THE "CAUSE" PRECEDING IT*:

$$I_1 \propto \vec{B}_1 \propto \Phi_2 \propto \frac{\Delta \Phi_2}{\Delta t} \propto \text{emf}_2 = V_2$$

- IN PARTICULAR:

$$\frac{\Delta I_1}{\Delta t} \propto V_2$$

"A CHANGE IN THE CURRENT THRU Loop #1 INDUCES A VOLTAGE ACROSS Loop #2."

- THE CONSTANT FOR THIS PROPORTIONALITY IS CALLED THE "MUTUAL INDUCTANCE" (M) OF LOOPS #1 & #2:



$$V_2 = M \frac{\Delta I_1}{\Delta t}$$

* THIS IS A RESULT OF THE SUPERPOSITION PRINCIPLE FOR ELEC. & MAG. FIELDS.


• MUTUAL INDUCTANCE

- M MEASURES HOW "RESPONSIVE" ONE COIL IS IN CHANGES IN THE OTHER :

LOW M :

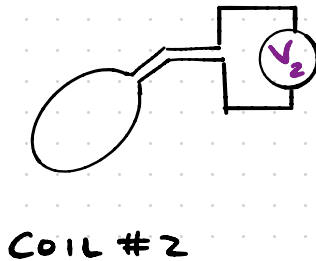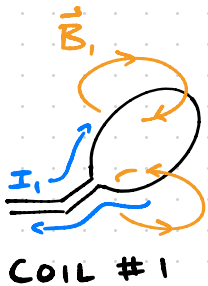


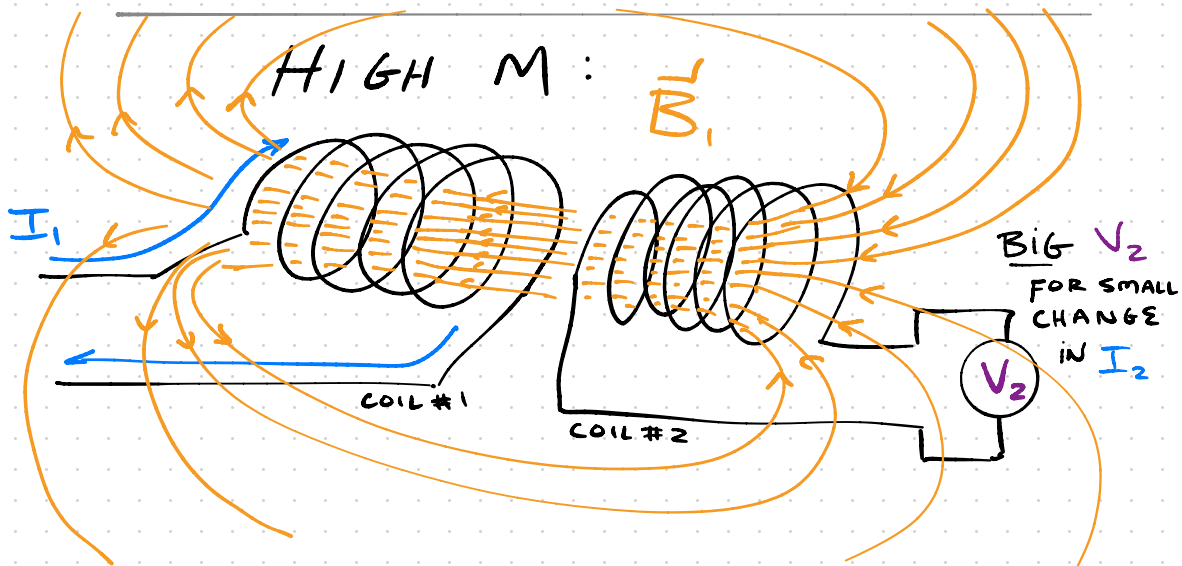COIL #2
CAN'T "DETECT"
CHANGES IN I_1
 $(V_2 = 0)$



SELF-INDUCTANCE

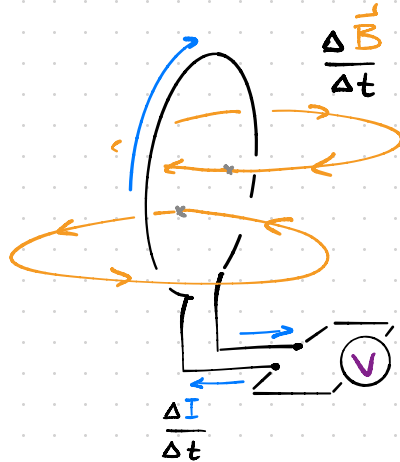- THIS "CHAIN OF INDUCTION" CAN OCCUR W/IN A SINGLE LOOP / COIL!



$$\frac{\Delta I}{\Delta t} \rightarrow \frac{\Delta \vec{B}}{\Delta t} \rightarrow \frac{\Delta \Phi}{\Delta t} \rightarrow \text{EMF} = \checkmark$$

- SO A LOOP / COIL HAS A "SELF-INDUCTANCE*" (L) SUCH THAT:

$$\checkmark = L \frac{\Delta I}{\Delta t}$$

- S.I. UNIT OF INDUCTANCE IS THE HENRY (H)

$$1 \text{ H} = 1 \frac{\text{V} \cdot \text{s}}{\text{A}}$$

* OR JUST "INDUCTANCE" FOR SHORT


• INDUCTANCES IN GENERAL

DIFFICULT TO CALCULATE,

BUT FOR A LONG, TIGHTLY-WOUND
COIL (AKA. A "SOLENOID")

WE HAVE:

$$L = \frac{\mu_0 N^2 A}{l}$$

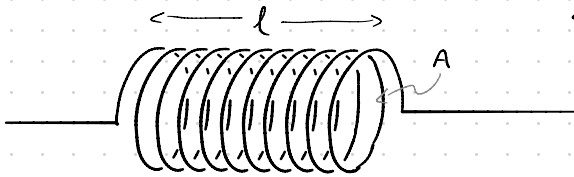

SOLENOID ($L \approx 1 \mu\text{H}$ IF TO SCALE)


$$\mu_0 = 1.257 \cdot 10^{-6} \text{ H/m}$$

N: # LOOPS

A: LOOP AREA


l: COIL LENGTH

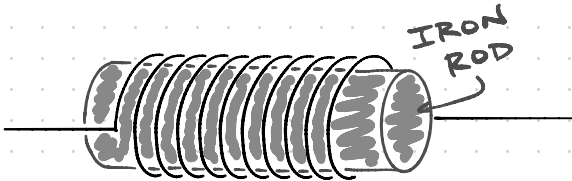- BY PUTTING IRON ROD INSIDE SOLENOID, CAN INCREASE INDUCTANCE BY $\approx 200,000 \times$!



$$L = \frac{\mu N^2 A}{l} \approx .2 \text{ H!} \left[\mu \approx 200,000 \times \mu_0 \text{ FOR IRON} \right]$$


INDUCTORS

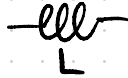- COILS w/ SIGNIFICANT INDUCTANCE.
- CIRCUIT DIAGRAM SYMBOL: 
- "OPPOSES SUDDEN CHANGES IN CURRENT."

RL CIRCUITS

- CONCEPTUALLY SIMILAR TO R.C. CIRCUITS.

— RL SERIES CIRCUIT

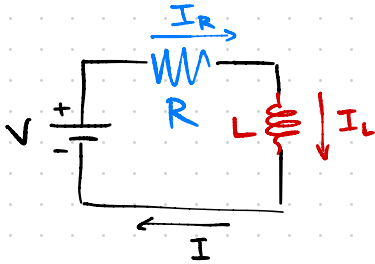

- Suppose @ $t=0$,
 $I=0$.
- WHAT HAPPENS AS
TIME GOES ON ($t > 0$)?

IN GENERAL:

- KCL: $I_R = I_L \equiv I$
- KVL: $V = V_R + V_L$

$$\textcircled{A} \quad V = IR + L \frac{\Delta I}{\Delta t}$$

@ $t=0$

- $I=0$
- $\textcircled{A} \quad V = \cancel{IR} + L \frac{\Delta I}{\Delta t}$
 $= L \frac{\Delta I}{\Delta t}$

→ $\frac{\Delta I}{\Delta t} = \frac{V}{L} \textcircled{B}$

AS $t \rightarrow \infty$:

• STEADY STATE

• NO CHANGING
VOLTAGES / CURRENTS

$$\rightarrow \frac{\Delta I}{\Delta t} = 0$$

• (A) $V = IR + L \frac{\Delta I}{\Delta t}$ ↗ (D)

→ $I = \frac{V}{R}$ (C)

IN BETWEEN

• AS CURRENT

BUILDS UP IN CIRCUIT:

• V_R INCREASES ($V_R = IR$)


• V_L DECREASES (KVL)

• $\frac{\Delta I}{\Delta t}$ DECREASES

(D) ($V_L = L \frac{\Delta I}{\Delta t}$)

$\frac{V}{R}$

$I(t)$


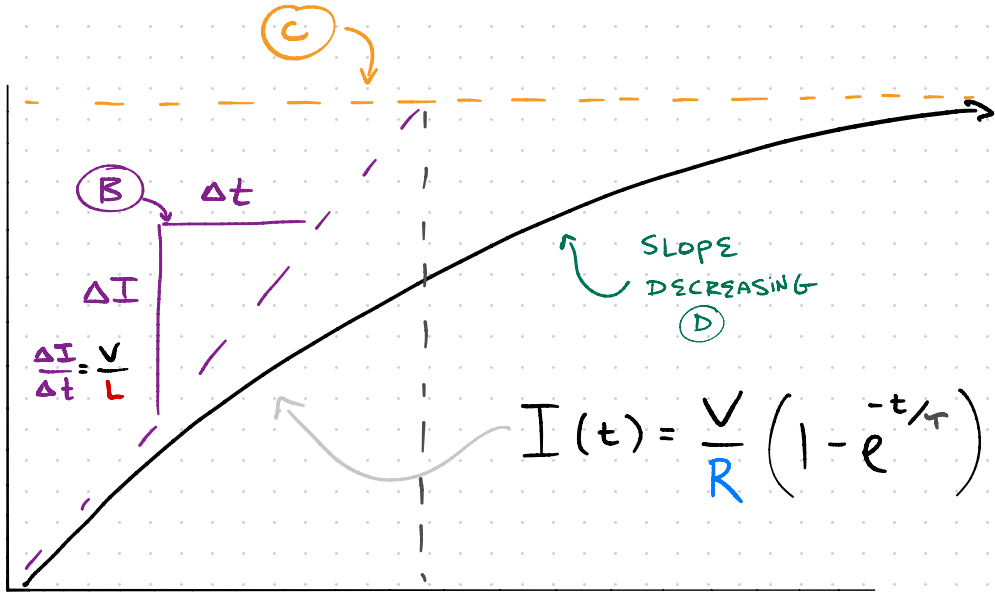


$\tau = L/R$

time



- SO CURRENT IN R.L. SERIES CIRCUIT "CHARGES UP" JUST LIKE CHARGE IN AN RC SERIES CIRCUIT :

RL :

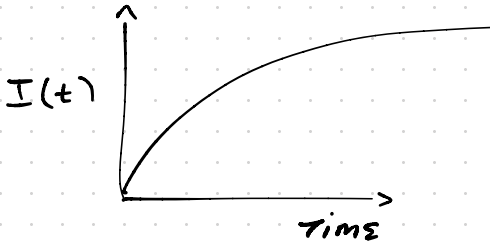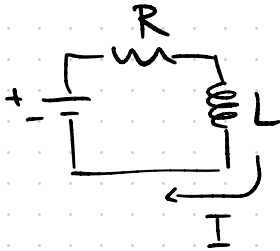

$$T = L/R$$

RC :

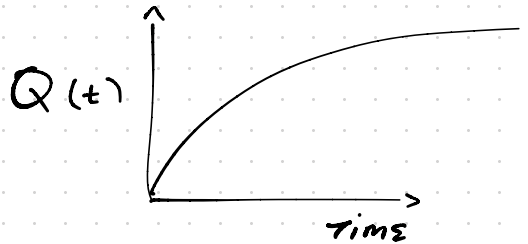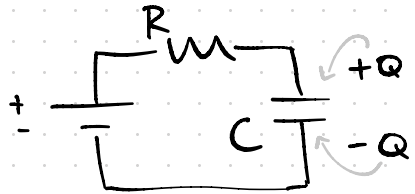


$$T = RC$$

• APPLICATION: FILTERING NOISE

- SUPPOSE WE WANT TO ELIMINATE NOISE FROM AN INPUT SIGNAL BEFORE SENDING IT TO AN OUTPUT:




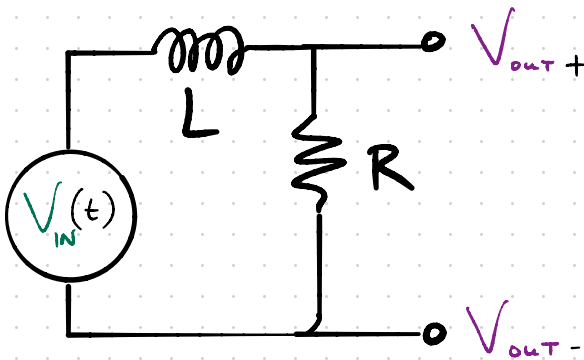- WE CAN ELIMINATE RAPIDLY VARYING NOISE (⚡), LEAVING ONLY THE SMOOTHLY VARYING SIGNAL (⤴) USING A "LOW-PASS" RL FILTER:




$$V_{OUT}(t) = V_{OUT+}(t) - V_{OUT-}(t) = V_R(t)$$

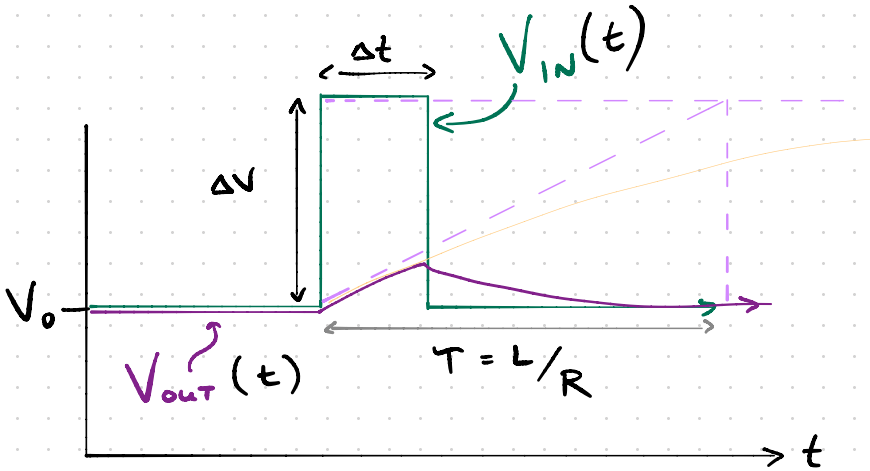- To SEE HOW THIS WORKS, LET'S CONSIDER A SIGNAL THAT IS A STEADY VOLTAGE V_0 AND "NOISE" CONSISTING OF A BUMP OF AMPLITUDE ΔV + DURATION Δt :



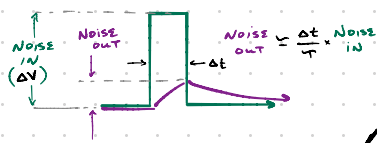- BECAUSE T MUCH LONGER THAN THAN Δt , CURRENT (AND THUS $V_R = IR$) DOES NOT GET FAR ALONG ITS "CHARGING CURVE" BEFORE NOISE Bump is OVER.



- NOISE Bump REDUCED BY FACTOR $\approx \frac{\Delta t}{T}$!