

INDUCTORS IN SERIES

* PARALLEL *

- TLDR : INDUCTORS COMBINE IN SERIES AND PARALLEL JUST LIKE RESISTORS :

SERIES

$$\text{---} \textcircled{L_1} \text{---} \textcircled{L_2} \text{---} = \text{---} \textcircled{L} \text{---}$$
$$L = L_1 + L_2$$

PARALLEL


$$\text{---} \textcircled{L_1} \text{---} \text{---} \textcircled{L_2} \text{---} = \text{---} \textcircled{L} \text{---}$$
$$L = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$

* THE INDUCTORS ARE ASSUMED TO BE FAR ENOUGH APART THAT THEIR MUTUAL INDUCTANCE (M) IS NEGLECTIBLE.

ARGUMENT :

SERIES : ——————
 L_1 L_2 ——————

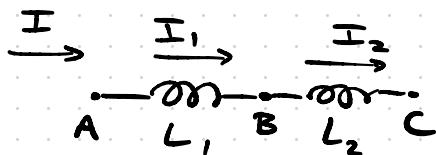- IF WE SEND IN A CURRENT CHANGING @ A RATE $\frac{\Delta I}{\Delta t}$,
WHAT IS THE VOLTAGE DROP OVER THE SERIES COMBINATION?



- KCL : $I_1 = I_2 = I$

$$\rightarrow \boxed{\frac{\Delta I_1}{\Delta t} = \frac{\Delta I_2}{\Delta t} = \frac{\Delta I}{\Delta t}}$$
A

- KVL : $V_{A \rightarrow C} = V_{A \rightarrow B \rightarrow C}$

$$\rightarrow V = V_1 + V_2$$

$$= L_1 \frac{\Delta I_1}{\Delta t} + L_2 \frac{\Delta I_2}{\Delta t}$$


(TRUE FOR ANY INDUCTOR)

$$= L_1 \frac{\Delta I}{\Delta t} + L_2 \frac{\Delta I}{\Delta t} \quad [\text{VIA } \textcolor{green}{A}]$$

$$= (L_1 + L_2) \frac{\Delta I}{\Delta t}$$

$$\rightarrow L = \underline{L_1 + L_2}$$

PARALLEL

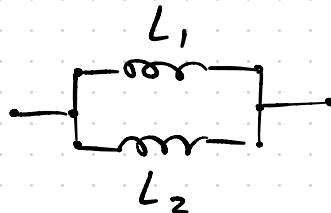

- IF WE MEASURE A VOLTAGE V ACROSS THE PARALLEL COMBO,

WHAT CAN WE DEDUCE ABOUT THE

RATE OF CHANGE $\frac{\Delta I}{\Delta t}$ OF CURRENT

THRU THE COMBO?

- KVL :

$$\begin{aligned} V_{A \rightarrow B} &= V_{A \rightarrow C \rightarrow D \rightarrow B} \\ &= V_{A \rightarrow E \rightarrow F \rightarrow B} \end{aligned}$$

$$\rightarrow V = V_1 = V_2$$


$$= L_1 \frac{\Delta I_1}{\Delta t} = L_2 \frac{\Delta I_2}{\Delta t}$$

- KCL :

$$I = I_1 + I_2$$

$$\rightarrow \frac{\Delta I}{\Delta t} = \frac{\Delta I_1}{\Delta t} + \frac{\Delta I_2}{\Delta t} = \frac{V}{L_1} + \frac{V}{L_2} = V \left(\frac{1}{L_1} + \frac{1}{L_2} \right)$$
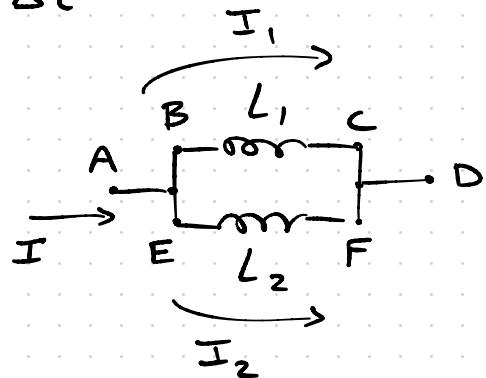
$$\rightarrow V = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1} \frac{\Delta I}{\Delta t} \rightarrow L = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$



$$\boxed{\begin{aligned} \frac{\Delta I_1}{\Delta t} &= V / L_1 \\ \frac{\Delta I_2}{\Delta t} &= V / L_2 \end{aligned}}$$

CONCEPTUALLY:

SERIES

- THE SAME CURRENT GOES THRU EACH, SO EMFs ADD.

PARALLEL

- CURRENT SPLITS, SO EMF ACROSS EITHER IS LESS THAN IF ENTIRE CURRENT WENT THRU ONE OR THE OTHER.