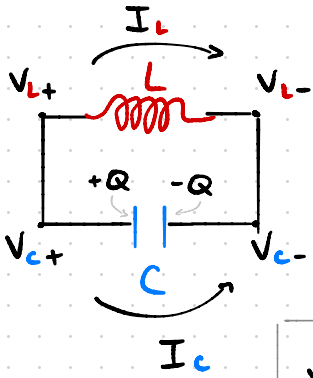


LC CIRCUITS

- LC "OSCILLATOR":



KVL:

$$V_L = V_{L+} - V_{L-} = V_{C+} - V_{C-} = V_C$$

KCL:


$$I_L = -I_C$$

$$V_L = L \frac{\Delta I_L}{\Delta t}, \quad V_C = \frac{Q}{C}, \quad I_C = \frac{\Delta Q}{\Delta t}$$

- COMBINING:

$$L \frac{\Delta I_C}{\Delta t} = -\frac{Q}{C}$$

- ANALOGY:

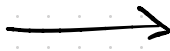

$$L \frac{\Delta I_C}{\Delta t} = -\frac{Q}{C} \quad \sim \quad ma = -kx$$

(LC OSCILLATOR) (Hooke's LAW)

Q
(CHARGE)

\sim

x
(POSITION)

$I_C = \frac{\Delta Q}{\Delta t}$
(CURRENT)

\sim

$v = \frac{\Delta x}{\Delta t}$
(VELOCITY)

$\frac{\Delta I_C}{\Delta t}$


\sim

$a = \frac{\Delta v}{\Delta t}$
(ACCELERATION)

COMPARING ABOVE:



$$L \sim m, \quad \frac{1}{C} \sim k$$

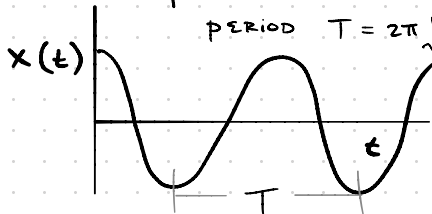SPRING OSCILLATES w/
PERIOD $T = 2\pi \sqrt{\frac{m}{k}}$



• By ANALOGY:

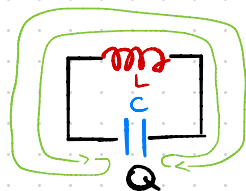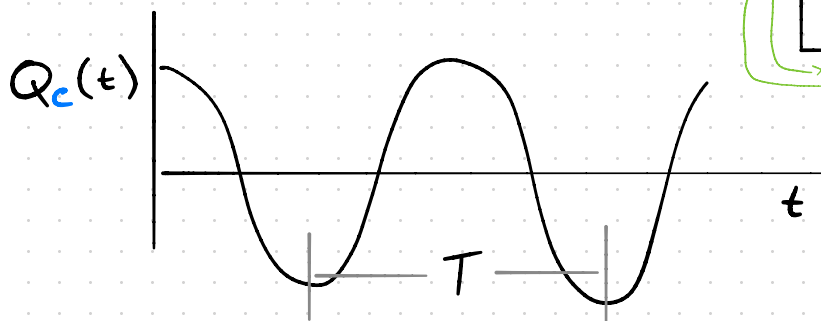CHARGE OSCILLATES BACK AND FORTH
BETWEEN TWO ENDS OF CAPACITOR
IN LC OSCILLATOR!



FOR SPRING:

$$T = 2\pi \sqrt{m/k}$$

SUBSTITUTING $m \rightarrow L$,
 $k \rightarrow 1/c$:



$$T = 2\pi \sqrt{L/1/c} = 2\pi \sqrt{LC} \quad \left[\begin{array}{l} \text{PERIOD OF OSCILLATION} \\ \text{IN LC OSCILLATOR} \end{array} \right]$$

$$f = \frac{1}{T} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \quad \left[\begin{array}{l} \text{"RESONANT FREQUENCY"} \end{array} \right]$$

GENERATION OF E.M. WAVES

- OSCILLATION OF CHARGE IN L.C. OSCILLATOR PRODUCES E.M. WAVES!

• I.E. THE OSCILLATOR "RADIATES".

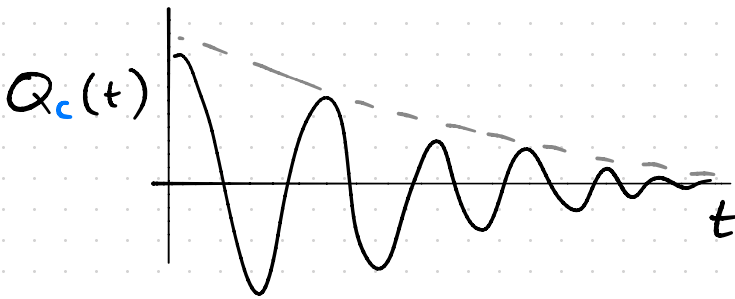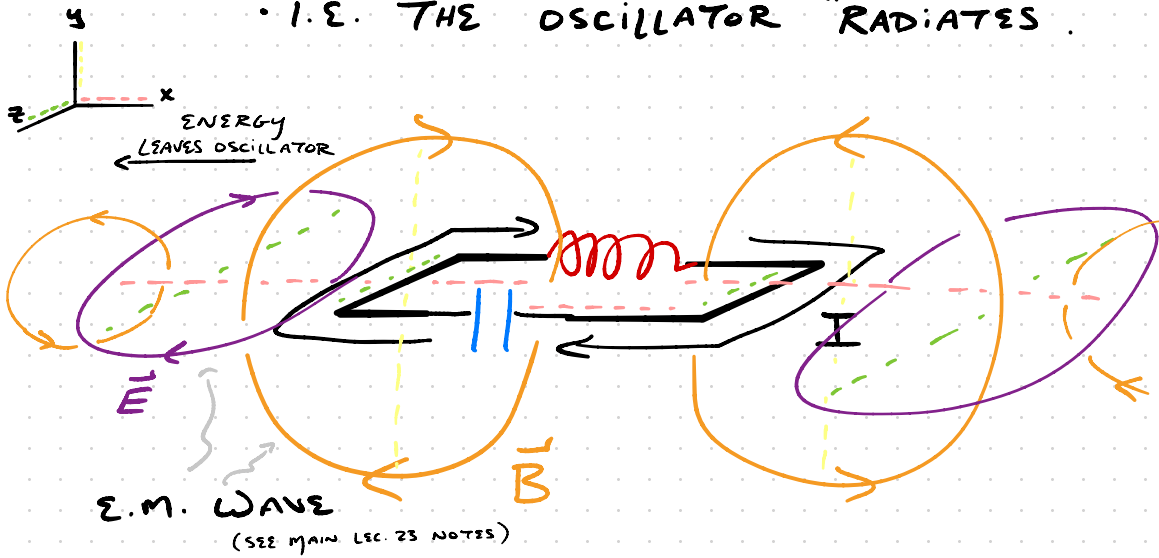

- ENERGY $E = \frac{1}{2} \frac{Q^2}{C}$ INITIALLY STORED ON CAPACITOR IS CONVERTED INTO E.M. WAVES!