
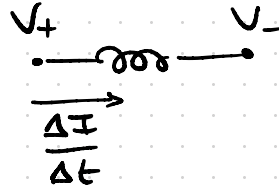


LECTURE 22 QUESTIONS




Q1 a) IF THE CURRENT THROUGH AN INDUCTOR IS INCREASING @ A RATE OF $1 \frac{\text{mA}}{\mu\text{s}}$, AND THE INDUCTOR HAS AN INDUCTANCE $L = 500 \mu\text{H}$, WHAT IS THE VOLTAGE ACROSS THE INDUCTOR?




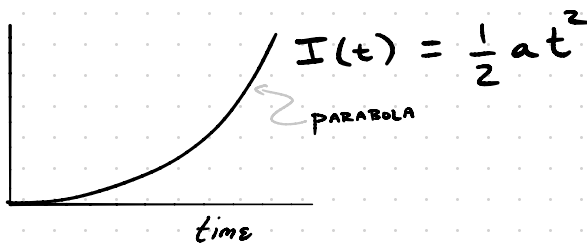b) BELOW IS THE PLOT OF THE CURRENT $I(t)$ THRU AN INDUCTOR VS. TIME.

PLOT THE VOLTAGE ACROSS THE INDUCTOR ON THE SAME GRAPH:



c) plot $V(t)$:

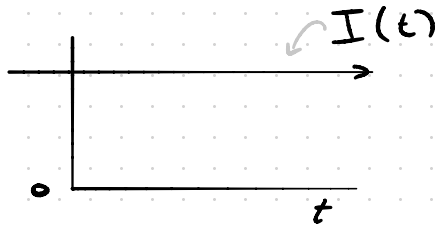

d) EXPLAIN HOW PART (c) DEMONSTRATES THE PRINCIPLE, "IN STEADY STATE AN INDUCTOR ACTS LIKE A SHORT-CIRCUIT."


e) IS THIS PRINCIPLE CONSISTENT W/ WHAT YOU KNOW INDUCTORS TO BE MADE OF?

BONUS: f) TWO INDUCTORS OF EQUAL INDUCTANCE ARE DRIVEN W/ A.C. CURRENTS OF EQUAL AMPLITUDES BUT DIFFERENT FREQUENCIES $f_1 < f_2$.

- WHICH HAS THE LARGER INDUCED VOLTAGE?

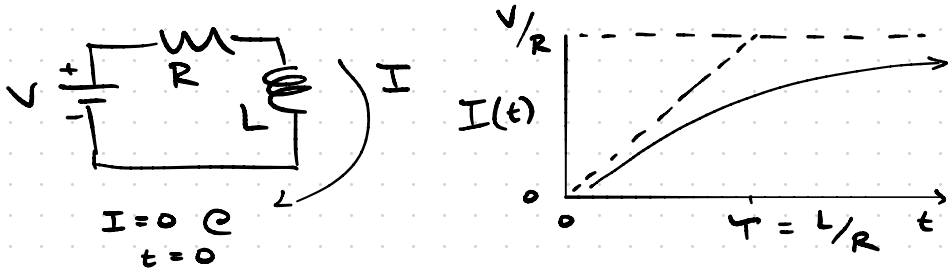Q2 SERIES RL SERIES CIRCUIT

REFER TO THE RESULT WORKED OUT FOR THE CURRENT IN THE RL SERIES CIRCUIT:



a) USE OHM'S LAW TO FIND:

- V_R @ $t = 0$
- V_R AS $t \rightarrow \infty$

b) USE K.V.L. TO FIND

- V_L @ $t = 0$
- * V_L AS $t \rightarrow \infty$


* IS THIS CONSISTENT W/ THE PRINCIPLE, STATED IN Q1, THAT,

"IN STEADY-STATE AN INDUCTOR ACTS LIKE A SHORT CIRCUIT."


* COMPARE THIS W/ THE PREDICTION FROM THE DEFINING RELATIONSHIP FOR AN INDUCTOR: $V = L \frac{\Delta I}{\Delta t}$

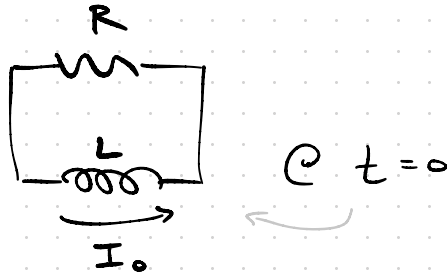Q3) DISCHARGING THE RL CIRCUIT

- @ TIME $t = 0$, SUPPOSE AN INDUCTOR IN AN INDUCTOR + RESISTOR COMBO CARRIES A CURRENT I_0 , AS SHOWN BELOW*:



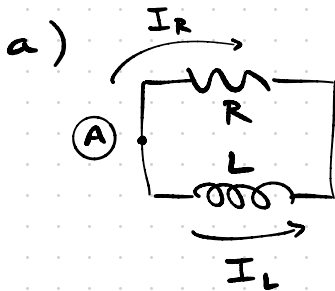- LET'S WORK OUT HOW THE INDUCTOR CURRENT CHANGES AS TIME GOES ON.




APPLY THE K.C.L.

@ THE NODE A TO SHOW THAT:

$$I_R = -I_L$$

* THIS COULD DESCRIBE, FOR INSTANCE, AN ALUMINUM RING W/ INDUCTANCE L & RESISTANCE R .

b)

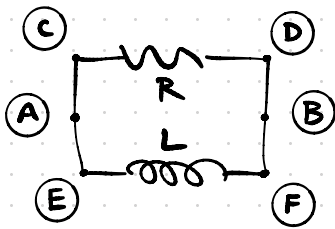

• USE THE K.V.L. FOR
THE PATHS $A \rightarrow C \rightarrow D \rightarrow B$
+ $A \rightarrow E \rightarrow F \rightarrow B$
TO SHOW THAT:

c) USE OHM'S LAW $V_R = V_L$
AND THE DEFINITION
OF INDUCTANCE TO SHOW THAT FROM (b):

$$I_R R = L \frac{\Delta I_L}{\Delta t}$$


d) COMBINE RESULT FROM PART a)
w/ RESULT FROM PART c)

TO SHOW: \textcircled{A}

$$\boxed{\frac{\Delta I_L}{\Delta t} = -\frac{I_L}{\tau}} \quad \text{WHERE } \tau = \frac{L}{R}$$

e) \textcircled{A} IS WHAT WE WILL NEED TO FIGURE
OUT $I_L(t)$ FOR $t > 0$. FOR STARTERS,
THOUGH, SIMPLY MAKE A POINT ON
THE I_L vs. t GRAPH FOR THE
INDUCTOR CURRENT I_L @ $t = 0$:
(SEE NEXT PAGE):

(e) CONT. : MARK $I_L(t)$ @ $t=0$:

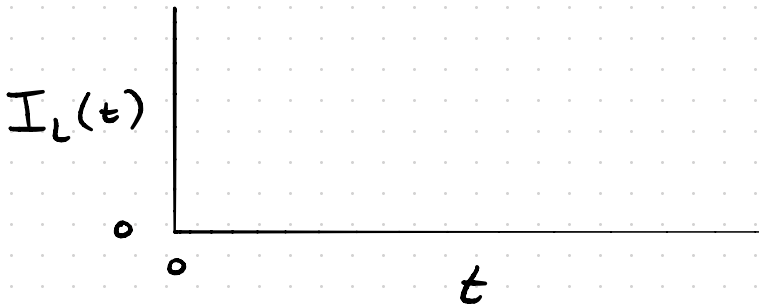

f) USING \textcircled{A} , ⁺ (e), DETERMINE THE RATE OF CHANGE $\frac{\Delta I_L}{\Delta t}$ @ $t=0$.

- NOTE THE SIGN OF THE SLOPE.
- DRAW A LINE STARTING FROM THE POINT YOU MARKED IN (e), EXTENDING TO THE HORIZONTAL (t) AXIS.
- WHERE DOES IT INTERSECT THE HORIZONTAL AXIS?

g) NOW, USE \textcircled{A} , ALONG W/ THE
"STEADY STATE CONDITION" (NO CHANGING
CURRENTS OR VOLTAGES), TO PREDICT THE
INDUCTOR CURRENT I_L AS $t \rightarrow \infty$.

- DRAW A HORIZONTAL LINE
THAT INTERSECTS THE VERTICAL
(I_L) AXIS AT THIS VALUE.

h) FINALLY, DRAW A SMOOTH CURVE THAT:

- STARTS @ THE POINT MARKED IN
STEP (e), THEN
- MOVES INITIALLY ALONG THE LINE
DRAWN IN PART (f), THEN:
- "PEELS OFF" THIS LINE, AND GRADUALLY
APPROACHES THE LINE FROM PART (g)
AS TIME GOES ON ($t \rightarrow \infty$).

(i) DO YOU RECALL THE NAME OF THIS CURVE? MATHEMATICALLY IT HAS THE FORM

$$I_L(t) = I_0 e^{-t/\tau}$$

- CHECK THAT THIS EQUATION AGREES W/ YOUR ANSWERS FOR PARTS (c) & (g), I.E. @ $t=0$ & $t \rightarrow \infty$.
- WHEN DOES THIS FORMULA PREDICT THAT $I_L(t)$ GOES TO $\frac{1}{e}$ OF ITS INITIAL VALUE? DOES THIS (ROUGHLY) AGREE W/ YOUR GRAPH?

$$(e = 2.72)$$

Bonus! • WHEN DOES $I_L(t)$ GO TO $\frac{1}{2}$ OF ITS INITIAL VALUE?

ANSWERS

Q1 a) $V = L \frac{\Delta I}{\Delta t}$

$$= 500 \cancel{\mu\text{H}} \cdot \frac{1 \text{ mA}}{\cancel{\mu\text{s}}}$$
$$= 500 \text{ mV}$$
$$= .5 \text{ V}$$

b) ANALOGY w PROJECTILE MOTION:


• IF $x(t) = \frac{1}{2} a t^2$

• THEN $v(t) = a t$


• SO IF $I(t) = \frac{1}{2} a t^2$

• THEN $\frac{\Delta I(t)}{\Delta t} = a t$
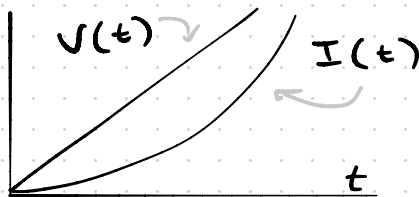
$$\rightarrow V(t) = L \frac{\Delta I(t)}{\Delta t} = L a t$$



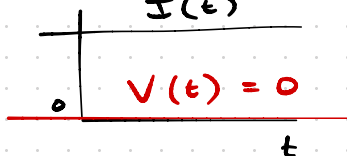
c) CURRENT CONSTANT $\rightarrow \frac{\Delta I}{\Delta t} = 0$



$$\rightarrow V = 0$$

d) IN (C) WE FIND THAT IN STEADY-STATE, WHERE CURRENTS ARE NOT CHANGING, THE VOLTAGE ACROSS AN INDUCTOR IS ZERO, NO MATTER WHAT (STEADY!) CURRENT CONDUCTS THRU IT. THIS " $V=0$ FOR ANY I " BEHAVIOR IS JUST HOW SHORT-CIRCUITS BEHAVE*.

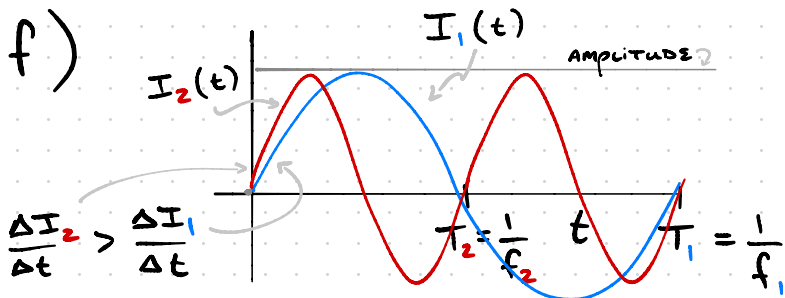e) WELL, INDUCTORS ARE MADE OF (CONDUCTING) WIRE, SO IT IS NOT SURPRISING THAT THEY ACT LIKE SHORT-CIRCUITS (WHEN CURRENT IS STEADY).



$$\rightarrow V_2 = L \frac{\Delta I_2}{\Delta t} > L \frac{\Delta I_1}{\Delta t} = V_1$$

Q2

FROM GRAPH:

- $I = 0$ @ $t = 0$ [OUR INITIAL ASSUMPTION]
- $I \rightarrow V/R$ AS $t \rightarrow \infty$ ["STEADY-STATE"]

a) FROM OHM'S LAW:

$$(V_R = IR)$$

- $V_R = (0) \times R = 0$ @ $t = 0$

- $V_R \rightarrow V/R \times R = V$ AS $t \rightarrow \infty$

b) K.V.L.: $V = V_R + V_L \rightarrow V_L = V - V_R$

SO: $V_L = V - (0) = V$ @ $t = 0$

- $V_L \rightarrow V - (V) = 0$ AS $t \rightarrow \infty$


* AGAIN WE SEE THAT VOLTAGE ACROSS INDUCTOR IS ZERO IN STEADY STATE, EVEN THOUGH CURRENT IS NON-ZERO ($I \rightarrow V/R$), I.E. INDUCTOR ACTS LIKE SHORT-CIRCUIT.

* WE ALSO SEE SLOPE OF $I(t)$ FLATTENING OUT AS $t \rightarrow \infty$, I.E. $\frac{\Delta I}{\Delta t} \rightarrow 0$. SO AGAIN WE FIND

$$V_L = L \frac{\Delta I}{\Delta t} \rightarrow 0 \text{ IN STEADY STATE.}$$

Q3

a)

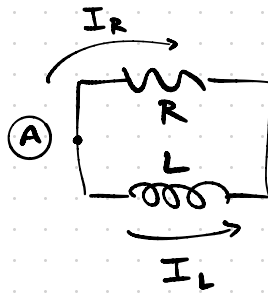

CURRENT INTO (A) = CURRENT OUT OF (A)


↓
0

↓
 $I_L + I_R$

=

→ $I_R = -I_L$ ✓

b)

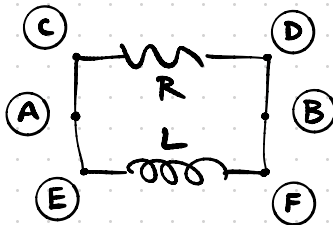

KVL: $V_{A \rightarrow C \rightarrow D \rightarrow B} = V_{A \rightarrow E \rightarrow F \rightarrow B}$

(WIRRES)

$V_{A \rightarrow C} + V_{C \rightarrow D} + V_{D \rightarrow B} = V_{A \rightarrow E} + V_{E \rightarrow F} + V_{F \rightarrow B}$

↓
 V_R

↓
 V_L

→ $V_R = V_L$ ✓

c) OHM'S LAW : $V_R = I_R R$

INDUCTORS : $V_L = L \frac{\Delta I_L}{\Delta t}$

$$I_R R = V_R = V_L = L \frac{\Delta I_L}{\Delta t} \quad \checkmark$$


(b)

d) PLUGGING IN [FROM (a)] $I_R = -I_L$
INTO (c) WE GET :


$$-I_L R = L \frac{\Delta I_L}{\Delta t}$$

$$\rightarrow \frac{\Delta I_L}{\Delta t} = -I_L \times \frac{R}{L} = \frac{-I_L}{L/R} = -\frac{I_L}{\tau} \quad \checkmark$$

e) By ASSUMPTION : $I = I_0$ @ $t = 0$

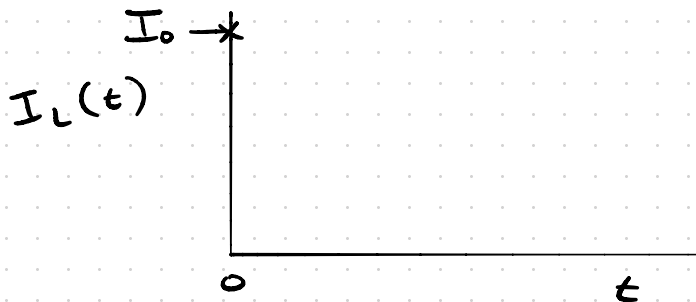

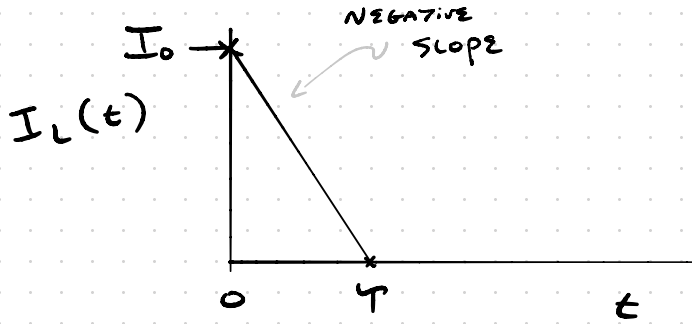
$$f) \quad \textcircled{A} \quad \frac{\Delta I_L}{\Delta t} = -\frac{I}{T} = -\frac{I_0}{T} \quad I_0 \text{ @ } t=0$$




g) STEADY-STATE: $\frac{\Delta I_L}{\Delta t} \rightarrow 0$

$$\rightarrow \textcircled{A} \quad \frac{\Delta I_L}{\Delta t} = -\frac{I}{T}$$

$$\rightarrow I \rightarrow 0$$

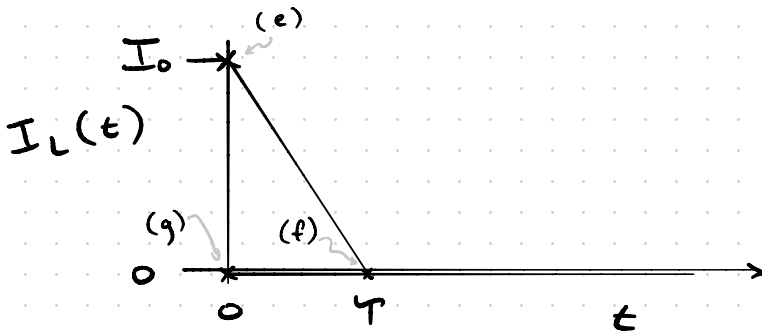

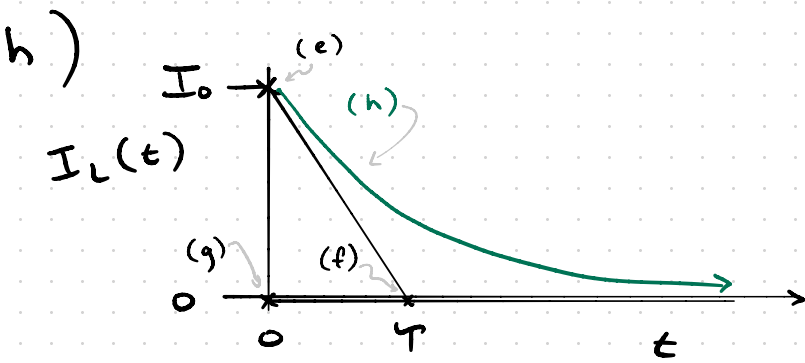


i) "EXPONENTIAL DECAY"

@ $t = 0$ $I(t=0) = I_0 e^{-0/\tau} = I_0 e^0 = I_0 \checkmark$

AS $t \rightarrow \infty$ $I(t \rightarrow \infty) = I_0 e^{-\infty/\tau} = I_0 \frac{1}{e^{\infty/\tau}} \rightarrow 0 \checkmark$

• I_L GOES TO $\frac{I_0}{e}$ @ $t = \tau$ (DENOM. GETS BIT!)
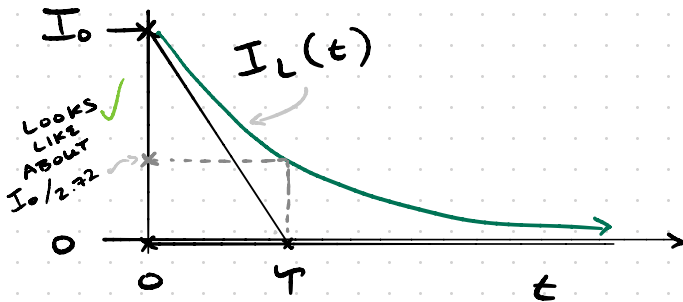
$$I(t = \tau) = I_0 e^{-\tau/\tau} = I_0 e^{-1} = \frac{I_0}{e} \approx \frac{I_0}{2.72}$$



• @ WHAT $t_{1/2}$ DOES $I(t) = I_0/2$?

$$I(t_{1/2}) = I_0 e^{-t_{1/2}/\tau} = I_0/2$$

$$\frac{I_0}{e^{t_{1/2}/\tau}} = \frac{I_0}{2}$$

$$\rightarrow e^{t_{1/2}/\tau} = 2$$

$$\ln(e^{t_{1/2}/\tau}) = \ln 2$$

$$t_{1/2}/\tau = \ln 2$$

$$t_{1/2} = \ln 2 \times \tau \approx .69\tau$$

